

Міністерство освіти і науки України
Національний університет “Львівська політехніка”
Кафедра ЕОМ



Звіт
про виконання лабораторної роботи №3
з дисципліни:
“Моделювання комп’ютерних систем”

Виконав: ст.гр. КІ-201
Голодняк А.Р.
Прийняв: асистент
Козак Н.Б.

Львів 2023

Тема роботи


Поведінковий опис цифрового автомата Перевірка роботи автомата за допомогою стенда Elbert V2- Spartan 3A FPGA.

Мета роботи

На базі стенда Elbert V2- Spartan 3A FPGA реалізувати цифровий автомат для обчислення значення виразу дотримуючись наступних вимог:

Інтерфейс пристрою та функціонал реалізувати згідно отриманого варіанту завдання.

1. Функціонал пристрою повинен бути реалізований згідно отриманого варіанту завдання Дивись розділ ЗАВДАННЯ
2. Пристрій повинен бути ітераційним АЛП повинен виконувати за один такт одну операцію та реалізованим згідно наступної структурної схеми
3. Кожен блок структурної схеми повинен бути реалізований на мові в окремому файлі Дозволено використовувати всі оператори
4. Для кожного блока структурної схеми повинен бути згенерований символ
5. Інтеграція структурних блоків в єдину систему та зі стендом повинна бути виконана за допомогою
6. Кожен структурний блок і схема в цілому повинні бути промодельовані за допомогою симулятора
7. Формування вхідних даних на шині повинно бути реалізовано за допомогою перемикачів елемент на стенді Див Додаток інформація про стенд наймолодший розряд значення операнду найстарший розряд значення операнду.
8. Керування пристроєм повинно бути реалізовано за допомогою кнопок елементи на стенді Див Додаток інформація про стенд запис першого операнду в пам'ять даних автомата запис другого операнду в пам'ять даних автомата запуск процесу обчислення скидання автомата у початковий стан
9. Індикація значень операндів при вводі та вивід результату обчислень повинні бути реалізовані за допомогою семи сегментних індикаторів Індикація переповнення в АЛП за допомогою на стенді Див Додаток інформація про стенд
10. Підготувати і захистити звіт

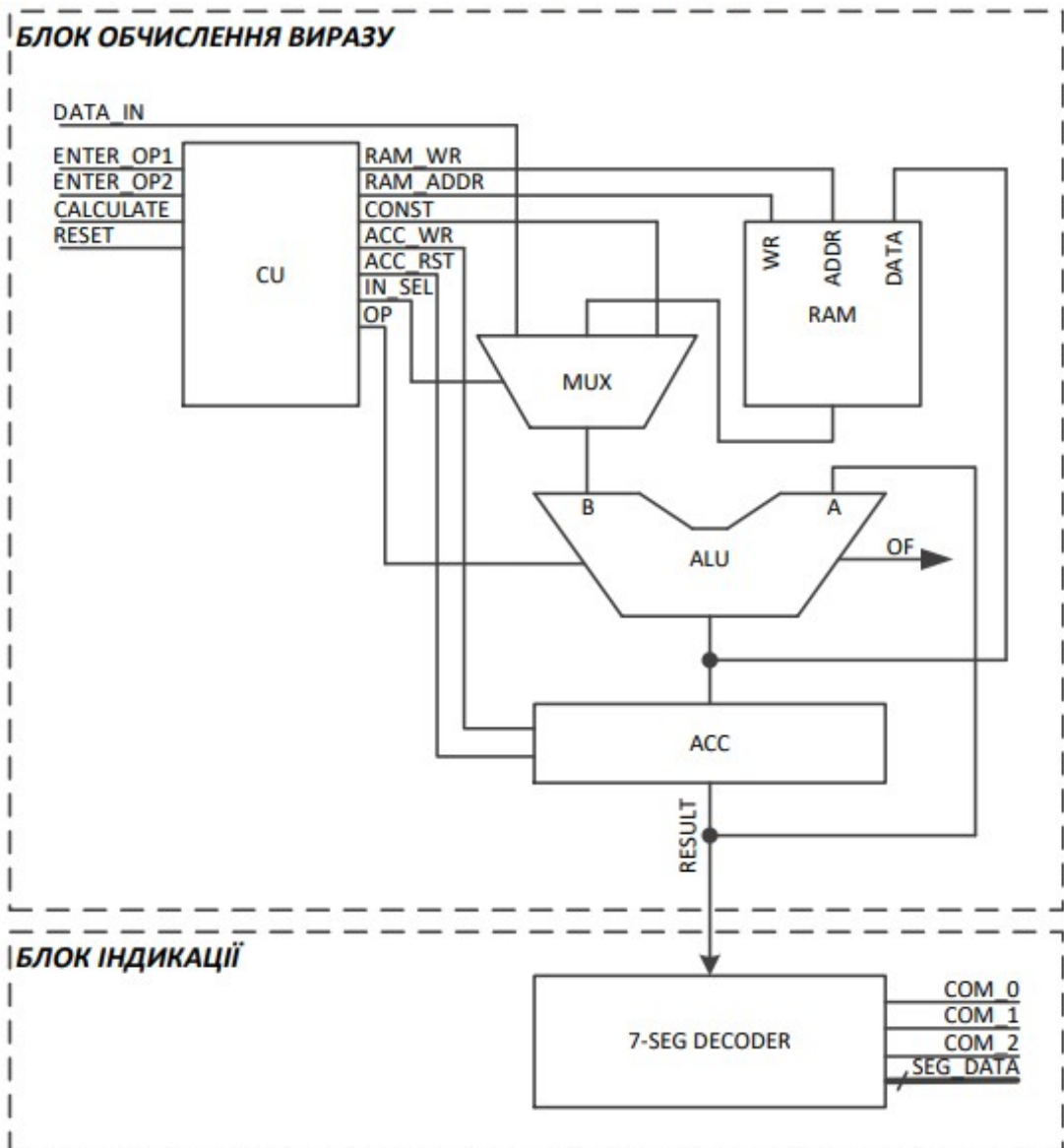

Малюнок 1 - Структурна схема автомата.

Виконання завдання

Мій варіант – 3.

ЗАВДАННЯ:

| ВАРІАНТ | ВИРАЗ |
|---------|--------------------------------------|
| 0 | $((OP1 - OP2) + 4) \ll OP2$ |
| 1 | $((OP1 + 2) * OP2) \ll OP1$ |
| 2 | $((OP1 \text{ or } OP2) + OP2) - 3$ |
| 3 | $((OP2 \text{ and } 5) + OP2) - OP1$ |
| 4 | $((4 + OP1) \text{ xor } OP2) - OP1$ |
| 5 | $((1 \ll OP1) + OP2) - OP1$ |
| 6 | $((OP1 + OP2) - 2) \ll OP2$ |
| 7 | $((OP1 \ll 2) - OP2) + 4$ |
| 8 | $((OP1 * OP2) \gg 1) + OP1$ |
| 9 | $((OP2 - 4) + OP1) \text{ or } 2$ |
| 10 | $((OP2 - OP1) \ll 1) + OP1$ |
| 11 | $((OP1 * 2) + OP2) \gg 1$ |
| 12 | $((OP1 \text{ xor } OP2) + OP2) - 1$ |

Таблиця 1 – Варіанти завдань.

Мій вираз : $((OP2 \text{ and } 5) + OP2) - OP1$

Виконання роботи:

1. Створив VHDL мультиплексор


```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity my_MuX_intf is
port(
    DATA_IN      : in std_logic_vector(7 downto 0);
    IN_SEL        : in std_logic_vector(1 downto 0);
    CONSTANT_BUS   : in std_logic_vector(7 downto 0);
    RAM_DATA_OUT_BUS : in std_logic_vector(7 downto 0);
    IN_SEL_OUT_BUS  : out std_logic_vector(7 downto 0)
);
end my_MuX_intf;

architecture my_MuX_arch of my_MuX_intf is

begin
    INSEL_A_MUX : process(DATA_IN, CONSTANT_BUS, RAM_DATA_OUT_BUS, IN_SEL)
    begin
        if(IN_SEL = "00") then
            IN_SEL_OUT_BUS <= DATA_IN;
        elsif(IN_SEL = "01") then
            IN_SEL_OUT_BUS <= RAM_DATA_OUT_BUS;
        else
            IN_SEL_OUT_BUS <= CONSTANT_BUS;
        end if;
    end process INSEL_A_MUX;
end my_MuX_arch;
```

2. Симуляція роботи мультиплексора

 

3. Створив VHDL файл який реалізує регістр ACC

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity my_ACC_intf is
port(
    CLOCK      : in std_logic;
    ACC_WR      : in std_logic;
    ACC_RST     : in std_logic;
    ACC_DATA_IN_BUS : in std_logic_vector(7 downto 0);
    ACC_DATA_OUT_BUS : out std_logic_vector(7 downto 0)
);
end my_ACC_intf;

architecture my_ACC_arch of my_ACC_intf is


    signal ACC_DATA : std_logic_vector(7 downto 0);

begin

    ACC : process(CLOCK, ACC_DATA)
    begin
        if (rising_edge(CLOCK)) then
            if(ACC_RST = '1') then
                ACC_DATA <= "00000000";
            elsif (ACC_WR = '1') then
                ACC_DATA <= ACC_DATA_IN_BUS;
            end if;
        end if;
        ACC_DATA_OUT_BUS <= ACC_DATA;
    end process ACC;

end my_ACC_arch;
```

4. Симуляція роботи регістра

 

5. Створив VHDL файл який реалізує ALU

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity my_ALU_intf is
port(
    OP_CODE_BUS : in std_logic_vector(1 downto 0);
    IN_SEL_OUT_BUS : in std_logic_vector(7 downto 0);
    ACC_DATA_OUT_BUS : in std_logic_vector(7 downto 0);
    ACC_DATA_IN_BUS : out std_logic_vector(7 downto 0)
);
end my_ALU_intf;
```

```

architecture my_ALU_arch of my_ALU_intf is

begin

    ALU : process(OP_CODE_BUS, IN_SEL_OUT_BUS, ACC_DATA_OUT_BUS)
        variable A : unsigned(7 downto 0);
        variable B : unsigned(7 downto 0);

        begin

            A := unsigned(ACC_DATA_OUT_BUS);
            B := unsigned(IN_SEL_OUT_BUS);


            case(OP_CODE_BUS) is
                when "00" => ACC_DATA_IN_BUS <= STD_LOGIC_VECTOR(B);
                when "01" => ACC_DATA_IN_BUS <= STD_LOGIC_VECTOR(A + B);
                when "10" => ACC_DATA_IN_BUS <= STD_LOGIC_VECTOR(A - B);
                when "11" => ACC_DATA_IN_BUS <= STD_LOGIC_VECTOR(B and "00000101");
                when others => ACC_DATA_IN_BUS <= "00000000";
            end case;

        end process ALU;

    end my_ALU_arch;

```

6. Симуляція роботи АЛП

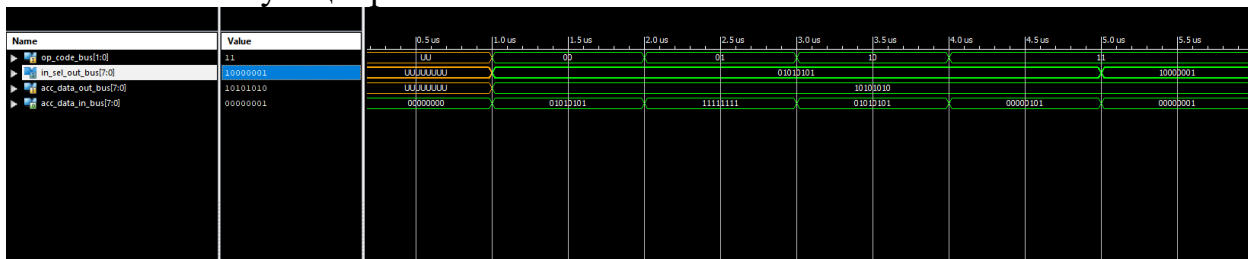

7. Створив VHDL файл який реалізує CU

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity my_CU_intf is
    port(
        CLOCK      : in std_logic;
        ENTER_OP1   : in std_logic;
        ENTER_OP2   : in std_logic;
        CALCULATE   : in std_logic;
        RESET       : in std_logic;

        RAM_WR      : out std_logic;
        RAM_ADDR_BUS : out std_logic_vector(1 downto 0);
        CONSTANT_BUS : out std_logic_vector(7 downto 0);
        ACC_WR      : out std_logic;
        ACC_RST     : out std_logic;
        IN_SEL      : out std_logic_vector(1 downto 0);
        OP_CODE_BUS : out std_logic_vector(1 downto 0)
    );
end my_CU_intf;

architecture my_CU_arch of my_CU_intf is

    type cu_state_type is (cu_rst, cu_idle, cu_load_op1, cu_load_op2, cu_run_calc0, cu_run_calc1, cu_run_calc2, cu_run_calc3, cu_finish);
    signal cu_cur_state : cu_state_type;

```

```
signal cu_next_state : cu_state_type;
```

```
begin
```

```
CONSTANT_BUS <= "00000001";
```

```
CU_SYNC_PROC: process (CLOCK)
```

```
begin
```

```
if (rising_edge(CLOCK)) then
```

```
if (RESET = '1') then
```

```
cu_cur_state <= cu_rst;
```

```
else
```

```
cu_cur_state <= cu_next_state;
```

```
end if;
```

```
end if;
```

```
end process;
```

```
CUNEXT_STATE_DECODE: process (cu_cur_state, ENTER_OP1, ENTER_OP2, CALCULATE)
```

```
begin
```

```
--declare default state for next_state to avoid latches
```

```
cu_next_state <= cu_cur_state; --default is to stay in current state
```

```
--insert statements to decode next_state
```

```
--below is a simple example
```

```
case(cu_cur_state) is
```

```
when cu_rst =>
```

```
cu_next_state <= cu_idle;
```

```
when cu_idle =>
```

```
if (ENTER_OP1 = '1') then
```

```
cu_next_state <= cu_load_op1;
```

```
elsif (ENTER_OP2 = '1') then
```

```
cu_next_state <= cu_load_op2;
```

```
elsif (CALCULATE = '1') then
```

```
cu_next_state <= cu_run_calc0;
```

```
else
```

```
cu_next_state <= cu_idle;
```

```
end if;
```

```
when cu_load_op1 =>
```

```
cu_next_state <= cu_idle;
```

```
when cu_load_op2 =>
```

```
cu_next_state <= cu_idle;
```

```
when cu_run_calc0 =>
```

```
cu_next_state <= cu_run_calc1;
```

```
when cu_run_calc1 =>
```

```
cu_next_state <= cu_run_calc2;
```

```
when cu_run_calc2 =>
```

```
cu_next_state <= cu_run_calc3;
```

```
when cu_run_calc3 =>
```

```
cu_next_state <= cu_finish;
```

```
when cu_finish =>
```

```
cu_next_state <= cu_finish;
```

```
when others =>
```

```
cu_next_state <= cu_idle;
```



```

end case;

end process;

```

```

CU_OUTPUT_DECODE: process (cu_cur_state)

```

```

begin

```

```

    case(cu_cur_state) is
        when cu_rst =>
            IN_SEL      <= "00";
            OP_CODE_BUS <= "00";
            RAM_ADDR_BUS <= "00";
            RAM_WR       <= '0';
            ACC_RST       <= '1';
            ACC_WR       <= '0';
        when cu_idle =>
            IN_SEL      <= "00";
            OP_CODE_BUS <= "00";
            RAM_ADDR_BUS <= "00";
            RAM_WR       <= '0';
            ACC_RST       <= '0';
            ACC_WR       <= '0';
        when cu_load_op1 =>
            IN_SEL      <= "00";
            OP_CODE_BUS <= "00";
            RAM_ADDR_BUS <= "00";
            RAM_WR       <= '1';
            ACC_RST       <= '0';
            ACC_WR       <= '1';
        when cu_load_op2 =>
            IN_SEL      <= "00";
            OP_CODE_BUS <= "00";
            RAM_ADDR_BUS <= "01";
            RAM_WR       <= '1';
            ACC_RST       <= '0';
            ACC_WR       <= '1';
        when cu_run_calc0 =>
            IN_SEL      <= "10";
            OP_CODE_BUS <= "00";
            RAM_ADDR_BUS <= "00";
            RAM_WR       <= '0';
            ACC_RST       <= '0';
            ACC_WR       <= '1';
        when cu_run_calc1 =>
            IN_SEL      <= "01";
            OP_CODE_BUS <= "11";
            RAM_ADDR_BUS <= "01";
            RAM_WR       <= '0';
            ACC_RST       <= '0';
            ACC_WR       <= '1';
        when cu_run_calc2 =>
            IN_SEL      <= "01";

```

```

        OP_CODE_BUS    <= "01";
        RAM_ADDR_BUS   <= "01";

        RAM_WR         <= '0';
        ACC_RST         <= '0';
        ACC_WR         <= '1';

    when cu_run_calc3 =>
        IN_SEL          <= "01";
        OP_CODE_BUS     <= "10";
        RAM_ADDR_BUS    <= "00";

        RAM_WR         <= '0';
        ACC_RST         <= '0';
        ACC_WR         <= '1';

    when cu_finish      =>
        IN_SEL          <= "00";
        OP_CODE_BUS     <= "00";
        RAM_ADDR_BUS    <= "00";

        RAM_WR         <= '0';
        ACC_RST         <= '0';
        ACC_WR         <= '0';

    when others          =>
        IN_SEL          <= "00";
        OP_CODE_BUS     <= "00";
        RAM_ADDR_BUS    <= "00";

        RAM_WR         <= '0';
        ACC_RST         <= '0';
        ACC_WR         <= '0';


end case;

end process;

end my_CU_arch;

```

8. Симуляція роботи керуючого автомата

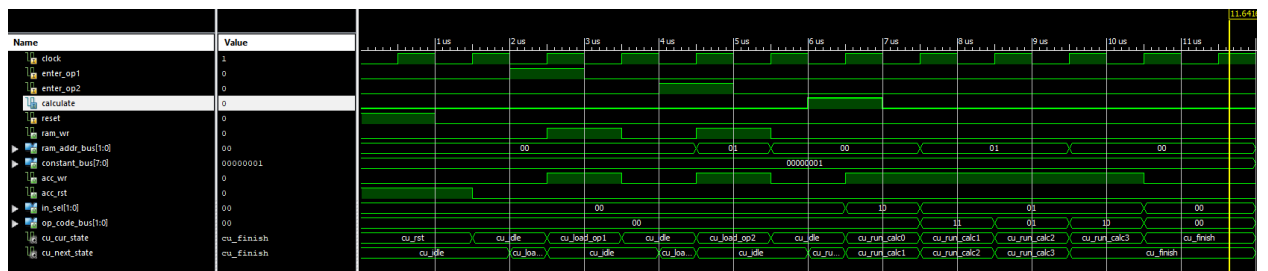

9. Створив VHDL файл який реалізує RAM

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity my_RAM_intf is
port(
    CLOCK      : in std_logic;
    RAM_WR      : in std_logic;
    RAM_ADDR_BUS : in STD_LOGIC_VECTOR(1 downto 0);
    RAM_DATA_IN_BUS : in STD_LOGIC_VECTOR(7 downto 0);
    RAM_DATA_OUT_BUS : out STD_LOGIC_VECTOR(7 downto 0)
);
end my_RAM_intf;


architecture my_RAM_arch of my_RAM_intf is

    type ram_type is array (3 downto 0) of STD_LOGIC_VECTOR(7 downto 0);
    signal RAM_UNIT : ram_type;

begin
    --when reset will init const
    RAM : process(CLOCK, RAM_ADDR_BUS, RAM_UNIT)
    begin
        if (rising_edge(CLOCK)) then
            if (RAM_WR = '1') then
                RAM_UNIT(conv_integer(RAM_ADDR_BUS)) <= RAM_DATA_IN_BUS;
            end if;
            RAM_DATA_OUT_BUS <= RAM_UNIT(conv_integer(RAM_ADDR_BUS));
        end process RAM;
    end my_RAM_arch;
end my_RAM_arch;

```

10. Симуляція роботи RAM

 

11. Створив VHDL файл який реалізує Sev_Seg_Decoder

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity OUT_PUT_DECODER_intf is
port(
    CLOCK      : IN STD_LOGIC;
    RESET      : IN STD_LOGIC;
    ACC_DATA_OUT_BUS : IN std_logic_vector(7 downto 0);

    COMM_ONES      : OUT STD_LOGIC;
    COMM_DECS      : OUT STD_LOGIC;
    COMM_HUNDREDS  : OUT STD_LOGIC;
    SEG_A          : OUT STD_LOGIC;
    SEG_B          : OUT STD_LOGIC;
    SEG_C          : OUT STD_LOGIC;

```

```

SEG_D                                : OUT STD_LOGIC;
SEG_E                                : OUT STD_LOGIC;
SEG_F                                : OUT STD_LOGIC;
SEG_G                                : OUT STD_LOGIC;
DP                                   : OUT STD_LOGIC
);
end OUT_PUT_DECODER_intf;

architecture OUT_PUT_DECODER_arch of OUT_PUT_DECODER_intf is
signal ONES_BUS : STD_LOGIC_VECTOR(3 downto 0) := "0000";
signal DECS_BUS : STD_LOGIC_VECTOR(3 downto 0) := "0001";
signal HONDREDS_BUS : STD_LOGIC_VECTOR(3 downto 0) := "0000";

begin

    BIN_TO_BCD : process (ACC_DATA_OUT_BUS)
        variable hex_src : STD_LOGIC_VECTOR(7 downto 0) ;
        variable bcd     : STD_LOGIC_VECTOR(11 downto 0) ;
    begin
        bcd      := (others => '0') ;
        hex_src   := ACC_DATA_OUT_BUS;

        for i in hex_src'range loop
            if bcd(3 downto 0) > "0100" then
                bcd(3 downto 0) := bcd(3 downto 0) + "0011" ;
            end if ;
            if bcd(7 downto 4) > "0100" then
                bcd(7 downto 4) := bcd(7 downto 4) + "0011" ;
            end if ;
            if bcd(11 downto 8) > "0100" then
                bcd(11 downto 8) := bcd(11 downto 8) + "0011" ;
            end if ;

            bcd := bcd(10 downto 0) & hex_src(hex_src'left) ; -- shift bcd + 1 new entry
            hex_src := hex_src(hex_src'left - 1 downto hex_src'right) & '0' ; -- shift src + pad with 0
        end loop ;

        HONDREDS_BUS    <= bcd (11 downto 8);
        DECS_BUS        <= bcd (7 downto 4);
        ONES_BUS        <= bcd (3 downto 0);

    end process BIN_TO_BCD;

    INDICATE : process(CLOCK)
        type DIGIT_TYPE is (ONES, DECS, HUNDREDS);

        variable CUR_DIGIT   : DIGIT_TYPE := ONES;
        variable DIGIT_VAL   : STD_LOGIC_VECTOR(3 downto 0) := "0000";
        variable DIGIT_CTRL  : STD_LOGIC_VECTOR(6 downto 0) := "0000000";
        variable COMMONS_CTRL : STD_LOGIC_VECTOR(2 downto 0) := "000";
    end process INDICATE;
end OUT_PUT_DECODER_arch;

```

```

begin
    if (rising_edge(CLOCK)) then
        if(RESET = '0') then
            case CUR_DIGIT is
                when ONES =>
                    DIGIT_VAL := ONES_BUS;
                    CUR_DIGIT := DECS;
                    COMMONS_CTRL := "001";

                when DECS =>
                    DIGIT_VAL := DECS_BUS;
                    CUR_DIGIT := HUNDREDS;
                    COMMONS_CTRL := "010";

                when HUNDREDS =>
                    DIGIT_VAL := HONDREDS_BUS;
                    CUR_DIGIT := ONES;
                    COMMONS_CTRL := "100";

                when others =>
                    DIGIT_VAL := ONES_BUS;
                    CUR_DIGIT := ONES;
                    COMMONS_CTRL := "000";

            end case;

            case DIGIT_VAL is
                --abcdefg
                when "0000" => DIGIT_CTRL := "1111110";
                when "0001" => DIGIT_CTRL := "0110000";
                when "0010" => DIGIT_CTRL := "1101101";
                when "0011" => DIGIT_CTRL := "1111001";
                when "0100" => DIGIT_CTRL := "0110011";
                when "0101" => DIGIT_CTRL := "1011011";
                when "0110" => DIGIT_CTRL := "1011111";
                when "0111" => DIGIT_CTRL := "1110000";
                when "1000" => DIGIT_CTRL := "1111111";
                when "1001" => DIGIT_CTRL := "1111011";
                when others => DIGIT_CTRL := "0000000";

            end case;

        else
            DIGIT_VAL := ONES_BUS;
            CUR_DIGIT := ONES;
            COMMONS_CTRL := "000";

        end if;

        COMM_ONES      <= COMMONS_CTRL(0);
        COMM_DECS      <= COMMONS_CTRL(1);
        COMM_HUNDREDS <= COMMONS_CTRL(2);

        SEG_A <= DIGIT_CTRL(6);
        SEG_B <= DIGIT_CTRL(5);
        SEG_C <= DIGIT_CTRL(4);
        SEG_D <= DIGIT_CTRL(3);
    end if;
end;

```

```

SEG_E <= DIGIT_CTRL(2);
SEG_F <= DIGIT_CTRL(1);
SEG_G <= DIGIT_CTRL(0);
DP      <= '0';


end if;

end process INDICATE;


end OUT_PUT_DECODER_arch;

```

12. Симуляція роботи декодера

 

13. Склав схему

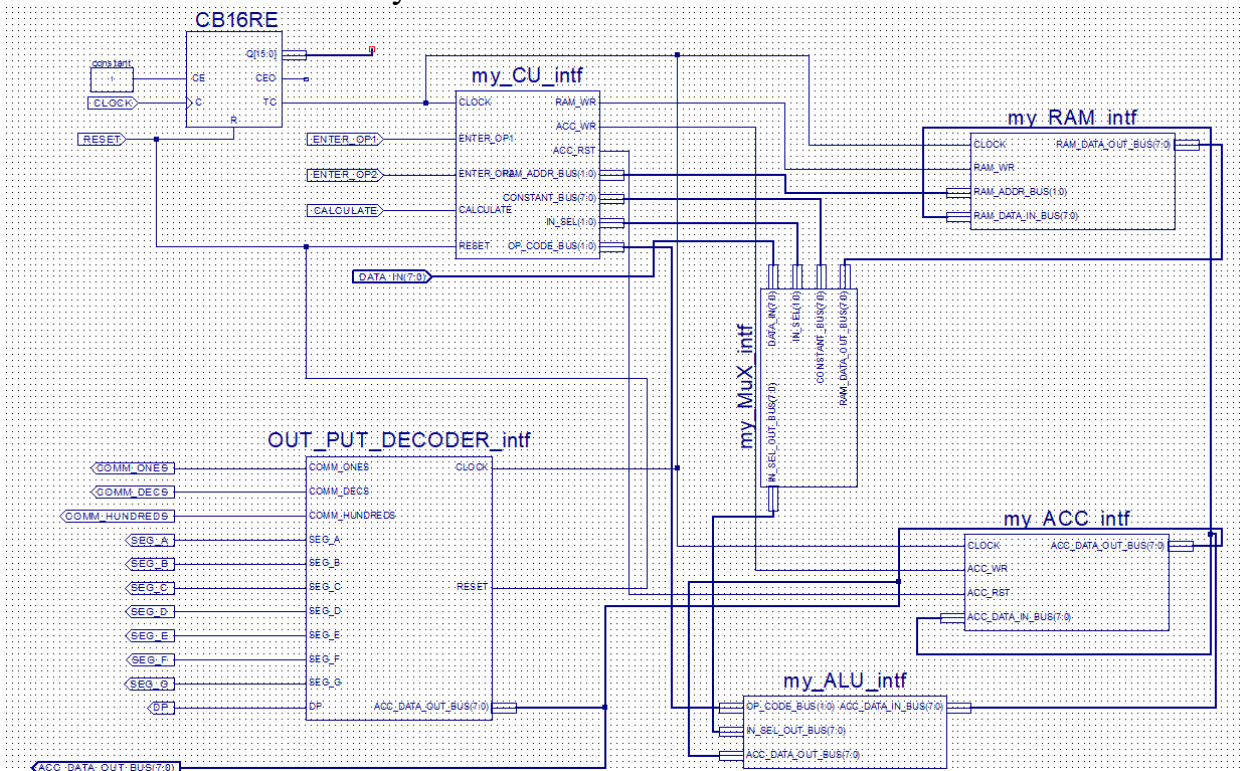


14. Симуляція роботи схеми

$$((\text{OP2 and 5}) + \text{OP2}) - \text{OP1}$$

При $OP1 = 0000\ 0100$, $OP2 = 0000\ 1011$;

0000 1011 and 101 = 0000 0001;
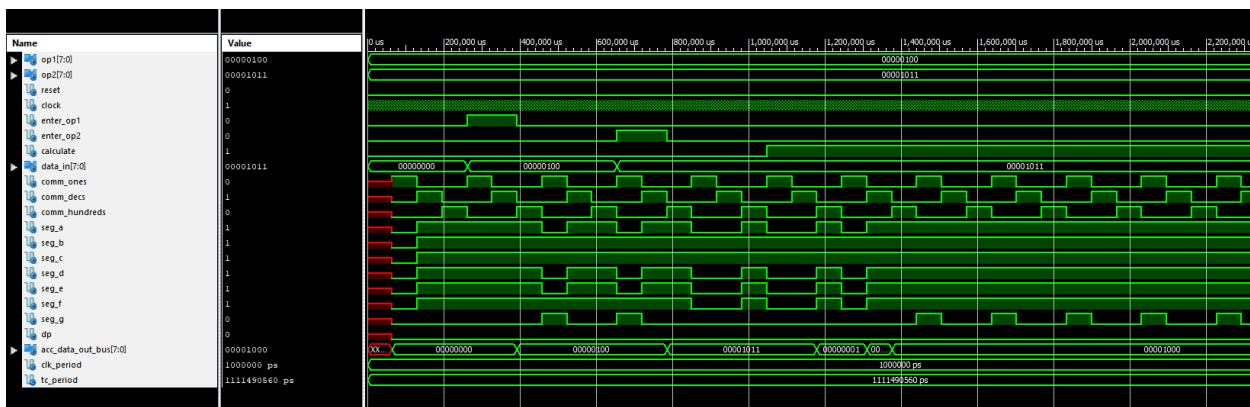
$$0000\ 0001 + 0000\ 1011 = 0000\ 1100;$$
$$0000\ 1100 - 0000\ 0100 = 0000\ 1000.$$


Висновок: На даній лабораторній роботі я на базі стенда Elbert V2-Spartan 3A FPGA реалізувати цифровий автомат для обчислення значення виразу.

