

Міністерство освіти і науки України
Національний університет „Львівська політехніка”
Кафедра ЕОМ



Звіт
з лабораторної роботи №2
з дисципліни: “Моделювання комп’ютерних систем”
на тему: “Структурний опис цифрового автомата”

Виконав:
ст. гр. КІ-201
Голодняк А.Р.

Прийняв:
Козак Н.Б.

Львів-2023

Мета: “На базі стенда реалізувати цифровий автомат світлових ефектів”.

Завдання до варіанту № 4:

Варіант – 4:

- Пристрій повинен реалізувати 8 комбінацій вихідних сигналів згідно таблиці:

Стан#	LED_0	LED_1	LED_2	LED_3	LED_4	LED_5	LED_6	LED_7
0	1	0	0	0	0	0	0	1
1	0	1	0	0	0	0	1	0
2	0	0	1	0	0	1	0	0
3	0	0	0	1	1	0	0	0
4	0	0	1	1	1	1	0	0
5	0	1	1	1	1	1	1	0
6	1	1	1	1	1	1	1	1
7	0	0	0	0	0	0	0	0

- Пристрій повинен використовувати 12MHz тактовий сигнал від мікроконтролера IC1 і знижувати частоту за допомогою внутрішнього подільника. Мікроконтролер IC1 є частиною стенда Elbert V2 – Spartan 3A FPGA. Тактовий сигнал заведено на вхід LOC = P129 FPGA (див. **Додаток – 1**).
- Інтерфейс пристрою повинен мати вхід синхронного скидання (RESET).
- Інтерфейс пристрою повинен мати вхід керування режимом роботи (MODE):
 - Якщо $MODE=0$ то стан пристрою інкрементується по зростаючому фронту тактового сигналу пам'яті станів (0->1->2->3->4->5->6->7->0...).
 - Якщо $MODE=1$ то стан пристрою декрементується по зростаючому фронту тактового сигналу пам'яті станів (0->7->6->5->4->3->2->1->0...).
- Інтерфейс пристрою повинен мати однорозрядний вхід керування швидкістю роботи (SPEED):
 - Якщо $SPEED=0$ то автомат працює зі швидкістю, визначеною за замовчуванням.
 - Якщо $SPEED=1$ то автомат працює зі швидкістю, **В 4 РАЗИ НИЖЧОЮ** ніж в режимі ($SPEED=0$).
- Для керування сигналом MODE використати будь який з 8 DIP перемикачів (див. **Додаток – 1**).
- Для керування сигналами RESET/SPEED використати будь які з PUSH BUTTON кнопок (див. **Додаток – 1**).

Хід виконання:


1) Створюю TransitionLogic.vhd

```
31
32 entity Transition_logic_intf is
33     Port ( CUR_STATE : in  std_logic_vector(2 downto 0);
34           MODE : in  std_logic;
35           NEXT_STATE : out std_logic_vector(2 downto 0)
36         );
37 end transition_logic_intf;
38
39 architecture transition_logic_arch of transition_logic_intf is
40
41 begin
42
43     NEXT_STATE(0) <= (not(MODE) and not(CUR_STATE(2)) and not (CUR_STATE(1)) and not (CUR_STATE(0))) or
44                     (not(MODE) and not(CUR_STATE(2)) and (CUR_STATE(1)) and not (CUR_STATE(0))) or
45                     (not(MODE) and (CUR_STATE(2)) and not (CUR_STATE(1)) and not (CUR_STATE(0))) or
46                     (not(MODE) and (CUR_STATE(2)) and (CUR_STATE(1)) and not (CUR_STATE(0))) or
47                     ( (MODE) and not(CUR_STATE(2)) and not (CUR_STATE(1)) and not (CUR_STATE(0))) or
48                     ( (MODE) and not(CUR_STATE(2)) and (CUR_STATE(1)) and not (CUR_STATE(0))) or
49                     ( (MODE) and (CUR_STATE(2)) and not (CUR_STATE(1)) and not (CUR_STATE(0))) or
50                     ( (MODE) and (CUR_STATE(2)) and (CUR_STATE(1)) and not (CUR_STATE(0)));
51
52     NEXT_STATE(1) <= (not(MODE) and not(CUR_STATE(2)) and not (CUR_STATE(1)) and (CUR_STATE(0))) or
53                     (not(MODE) and not(CUR_STATE(2)) and (CUR_STATE(1)) and not (CUR_STATE(0))) or
54                     (not(MODE) and (CUR_STATE(2)) and not (CUR_STATE(1)) and (CUR_STATE(0))) or
55                     (not(MODE) and (CUR_STATE(2)) and (CUR_STATE(1)) and not (CUR_STATE(0))) or
56                     ( (MODE) and not(CUR_STATE(2)) and not (CUR_STATE(1)) and not (CUR_STATE(0))) or
57                     ( (MODE) and not(CUR_STATE(2)) and (CUR_STATE(1)) and (CUR_STATE(0))) or
58                     ( (MODE) and (CUR_STATE(2)) and not (CUR_STATE(1)) and not (CUR_STATE(0))) or
59                     ( (MODE) and (CUR_STATE(2)) and (CUR_STATE(1)) and (CUR_STATE(0)));
60
61     NEXT_STATE(2) <= (not(MODE) and not(CUR_STATE(2)) and (CUR_STATE(1)) and (CUR_STATE(0))) or
62                     (not(MODE) and (CUR_STATE(2)) and not (CUR_STATE(1)) and not (CUR_STATE(0))) or
63                     (not(MODE) and (CUR_STATE(2)) and (CUR_STATE(1)) and not (CUR_STATE(0))) or
64                     (not(MODE) and (CUR_STATE(2)) and (CUR_STATE(1)) and not (CUR_STATE(0))) or
65                     ( (MODE) and not(CUR_STATE(2)) and not (CUR_STATE(1)) and not (CUR_STATE(0))) or
66                     ( (MODE) and not(CUR_STATE(2)) and (CUR_STATE(1)) and not (CUR_STATE(0))) or
67                     ( (MODE) and (CUR_STATE(2)) and (CUR_STATE(1)) and not (CUR_STATE(0))) or
68                     ( (MODE) and (CUR_STATE(2)) and (CUR_STATE(1)) and (CUR_STATE(0)));
69
70 end transition_logic_arch;
```


2) Створюю OutputLogic.vhd

```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3
4 entity out_logic_intf is
5     Port ( IN_BUS : in  std_logic_vector(2 downto 0);
6           OUT_BUS : out std_logic_vector(7 downto 0)
7         );
8 end out_logic_intf;
9
10 architecture out_logic_arch of out_logic_intf is
11
12 begin
13
14     OUT_BUS(0) <= (not(IN_BUS(2)) and not(IN_BUS(1)) and not(IN_BUS(0))) or
15                 (IN_BUS(2) and IN_BUS(1) and not(IN_BUS(0)));
16     OUT_BUS(1) <= (not(IN_BUS(2)) and not(IN_BUS(1)) and IN_BUS(0)) or
17                 (IN_BUS(2) and not(IN_BUS(1)) and IN_BUS(0)) or
18                 (IN_BUS(2) and IN_BUS(1) and not(IN_BUS(0)));
19     OUT_BUS(2) <= (not(IN_BUS(2)) and IN_BUS(1) and not(IN_BUS(0))) or
20                 (IN_BUS(2) and not(IN_BUS(1)) and not(IN_BUS(0))) or
21                 (IN_BUS(2) and not(IN_BUS(1)) and IN_BUS(0)) or
22                 (IN_BUS(2) and IN_BUS(1) and not(IN_BUS(0)));
23     OUT_BUS(3) <= (not(IN_BUS(2)) and IN_BUS(1) and IN_BUS(0)) or
24                 (IN_BUS(2) and not(IN_BUS(1)) and not(IN_BUS(0))) or
25                 (IN_BUS(2) and not(IN_BUS(1)) and IN_BUS(0)) or
26                 (IN_BUS(2) and IN_BUS(1) and not(IN_BUS(0)));
27     OUT_BUS(4) <= (not(IN_BUS(2)) and IN_BUS(1) and IN_BUS(0)) or
28                 (IN_BUS(2) and not(IN_BUS(1)) and not(IN_BUS(0))) or
29                 (IN_BUS(2) and not(IN_BUS(1)) and IN_BUS(0)) or
30                 (IN_BUS(2) and IN_BUS(1) and not(IN_BUS(0)));
31     OUT_BUS(5) <= (not(IN_BUS(2)) and IN_BUS(1) and not(IN_BUS(0))) or
32                 (IN_BUS(2) and not(IN_BUS(1)) and not(IN_BUS(0))) or
33                 (IN_BUS(2) and not(IN_BUS(1)) and IN_BUS(0)) or
34                 (IN_BUS(2) and IN_BUS(1) and not(IN_BUS(0)));
35     OUT_BUS(6) <= (not(IN_BUS(2)) and not(IN_BUS(1)) and IN_BUS(0)) or
36                 (IN_BUS(2) and not(IN_BUS(1)) and IN_BUS(0)) or
37                 (IN_BUS(2) and IN_BUS(1) and not(IN_BUS(0)));
38     OUT_BUS(7) <= (not(IN_BUS(2)) and not(IN_BUS(1)) and not(IN_BUS(0))) or
39                 (IN_BUS(2) and IN_BUS(1) and not(IN_BUS(0)));
40 end out_logic_arch;
```

3) Створюю схему LightController.sch

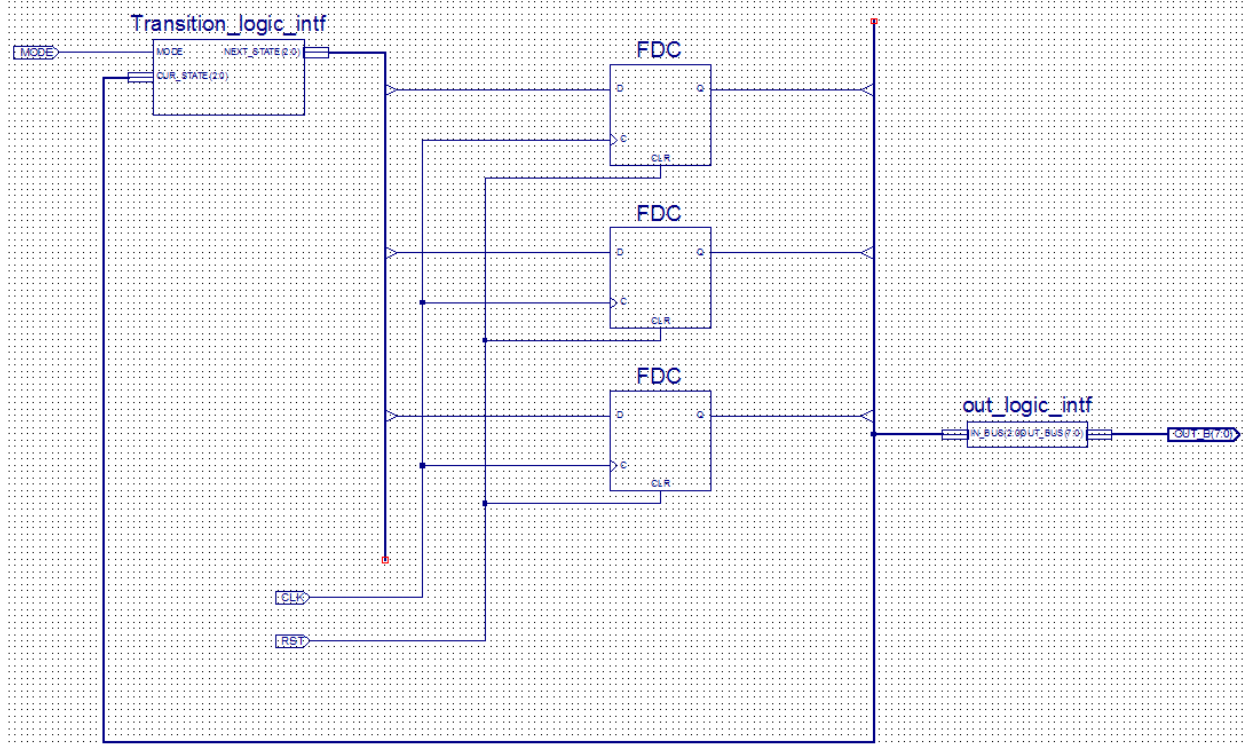

4) Створюю файл TopLevel.sch

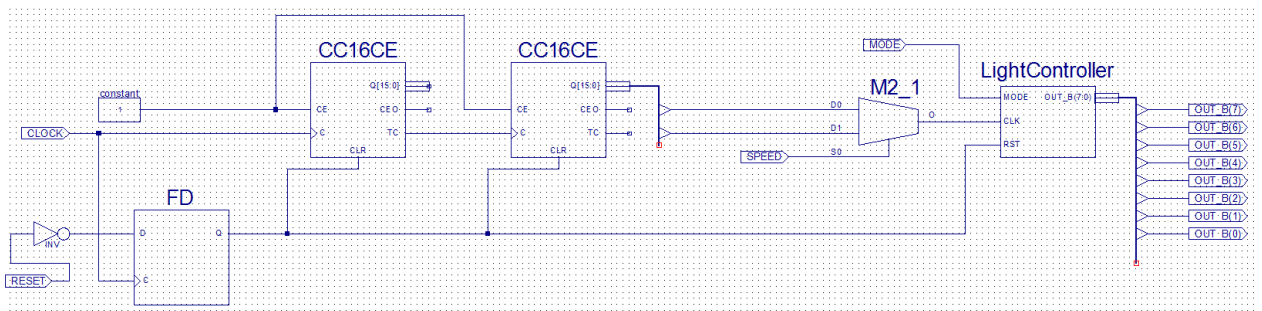

Також, щоб забезпечити можливість зменшення вхідної частоти в чотири рази – умова завдання, додаю мультіплексор.


5) Добавлю Constraints.ucf файл

```


7
8 #*****
9 #
10 #***** UCF for ElbertV2 Development Board *****
11 CONFIG VCCAUX = "3.3" ;
12
13 # Clock 12 MHz
14 NET "CLOCK" LOC = P129 | IOSTANDARD = LVCMOS33 | PERIOD = 12MHz;
15
16 #*****
17 # LED
18 #*****
19
20 NET "OUT_B(7)" LOC = P46 | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
21 NET "OUT_B(6)" LOC = P47 | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
22 NET "OUT_B(5)" LOC = P48 | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
23 NET "OUT_B(4)" LOC = P49 | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
24 NET "OUT_B(3)" LOC = P50 | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
25 NET "OUT_B(2)" LOC = P51 | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
26 NET "OUT_B(1)" LOC = P54 | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
27 NET "OUT_B(0)" LOC = P55 | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
28
29 #*****
30 # DP Switches
31 #*****
32
33 NET "MODE" LOC = P70 | PULLUP | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
34
35 #*****
36 # Switches
37 #*****
38 NET "RESET" LOC = P80 | PULLUP | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
39 NET "SPEED" LOC = P79 | PULLUP | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
40

```


6) Симулюю работу OutputLogic :

 


7) Симулюю работу TransitionLogic :

 


8) Симулюю роботу LightController.sch :

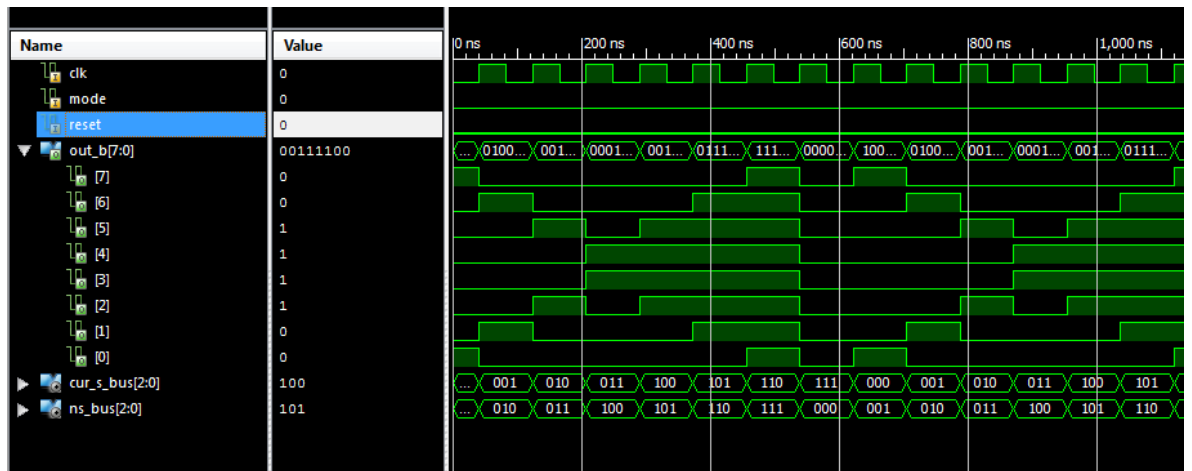

9) Симулюю роботу TopLevel.sch :

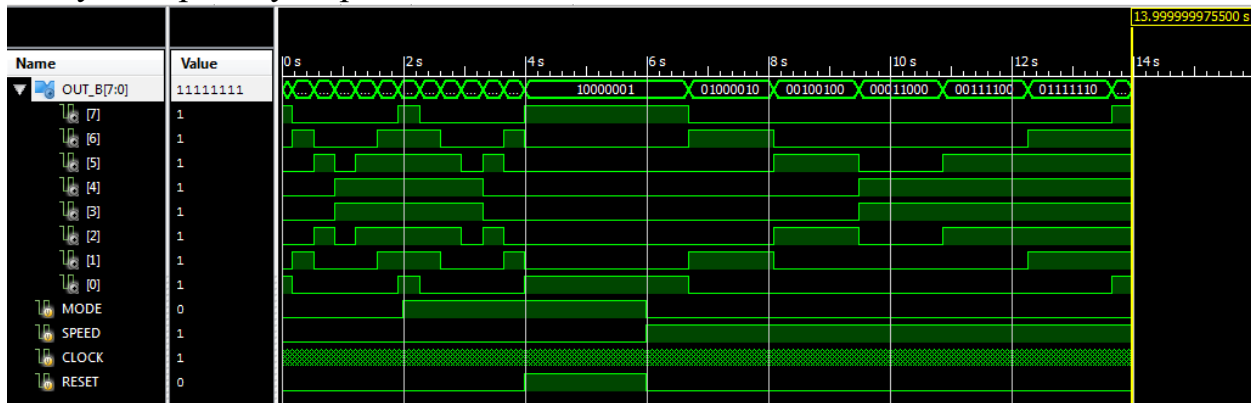

10) Генерую BIN файл :

 

Висновок: На даній лабораторній роботі я на базі стенда Elbert V2- Spartan 3A FPGA реалізував цифровий автомат світлових ефектів. Навчився створювати нові елементи і описувати логіку їх роботи засобами VHDL.